

Lab 01-gates


My repository

[My git - Tomáš Kříčka, 223283](#)

De Morgan's laws

c	b	a	f(c,b,a)
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	0

Waveforms

 

VHDL code

```

-----
--
-- Example of basic OR, AND, XOR gates.
-- Nexys A7-50T, Vivado v2020.1, EDA Playground
--
-- Copyright (c) 2019-2020 Tomas Fryza
-- Dept. of Radio Electronics, Brno University of Technology, Czechia
-- This work is licensed under the terms of the MIT license.
--
-----

library ieee;                -- Standard library

```

```

use ieee.std_logic_1164.all;-- Package for data types and logic operations

-----
-- Entity declaration for basic gates
-----
entity gates is
  port(
    a_i    : in  std_logic;      -- Data input
    b_i    : in  std_logic;      -- Data input
    c_i    : in  std_logic;
    f_o    : out std_logic;
    fnand_o : out std_logic;
    fnor_o  : out std_logic
    --for_o  : out std_logic;      -- OR output function
    --fand_o : out std_logic;      -- AND output function
    --fxor_o : out std_logic      -- XOR output function
  );
end entity gates;

-----
-- Architecture body for basic gates
-----
architecture dataflow of gates is
begin
  f_o <= ((not b_i) and a_i) or ((not c_i) and (not b_i));
  fnand_o <= ((b_i nand b_i) nand a_i) nand ((c_i nand c_i) nand (b_i nand
b_i));
  fnor_o <= (((a_i nor a_i) nor b_i) nor (b_i nor c_i)) nor (((a_i nor a_i) nor
b_i) nor (b_i nor c_i));

  --for_o  <= a_i or b_i;
  --fand_o <= a_i and b_i;
  --fxor_o <= a_i xor b_i;

end architecture dataflow;


```

[Link](#)

[Playground EDA](#)

Distributive laws

Waveforms

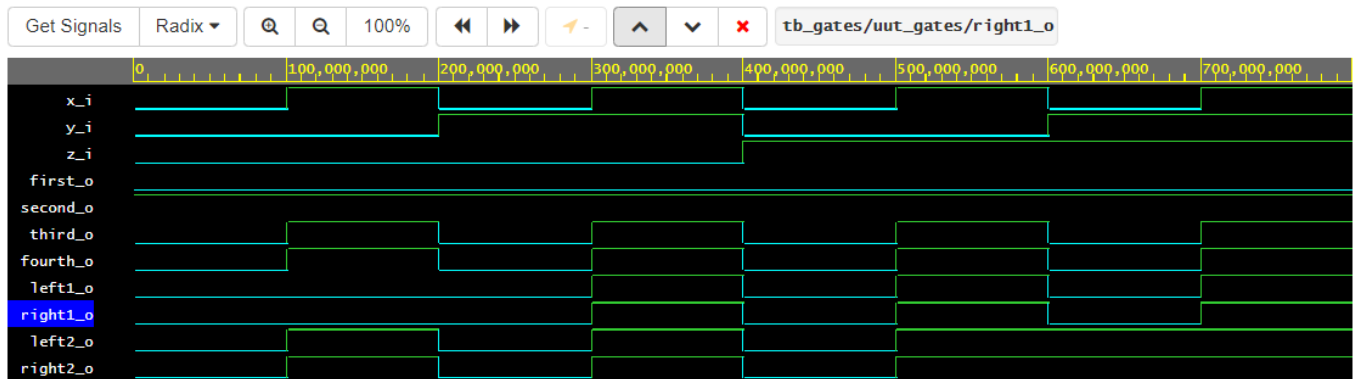

VHDL code

```
-- Code your design here
library IEEE;
use IEEE.std_logic_1164.all;

-----
-- Entity declaration for basic gates
-----

entity gates is
    port (
        x_i      : in std_logic;    -- input data
        y_i      : in std_logic;
        z_i      : in std_logic;

        first_o   : out std_logic;
        second_o  : out std_logic;
        third_o   : out std_logic;
        fourth_o  : out std_logic;

        left1_o   : out std_logic;
        right1_o  : out std_logic;
        left2_o   : out std_logic;
        right2_o  : out std_logic
    );
end entity gates;

-----
-- Architecture body for basic gates
-----

architecture dataflow of gates is
begin
    first_o <= x_i and not(x_i);
    second_o <= x_i or not(x_i);
    third_o <= x_i or x_i or x_i;
    fourth_o <= x_i and x_i and x_i;
```

```
left1_o <= (x_i and y_i) or (x_i and z_i);  
right1_o <= x_i and (y_i or z_i);  
left2_o <= (x_i or y_i) and (x_i or z_i);  
right2_o <= x_i or (y_i and z_i);
```

```
end architecture dataflow;
```

Link

[Playground EDA](#)