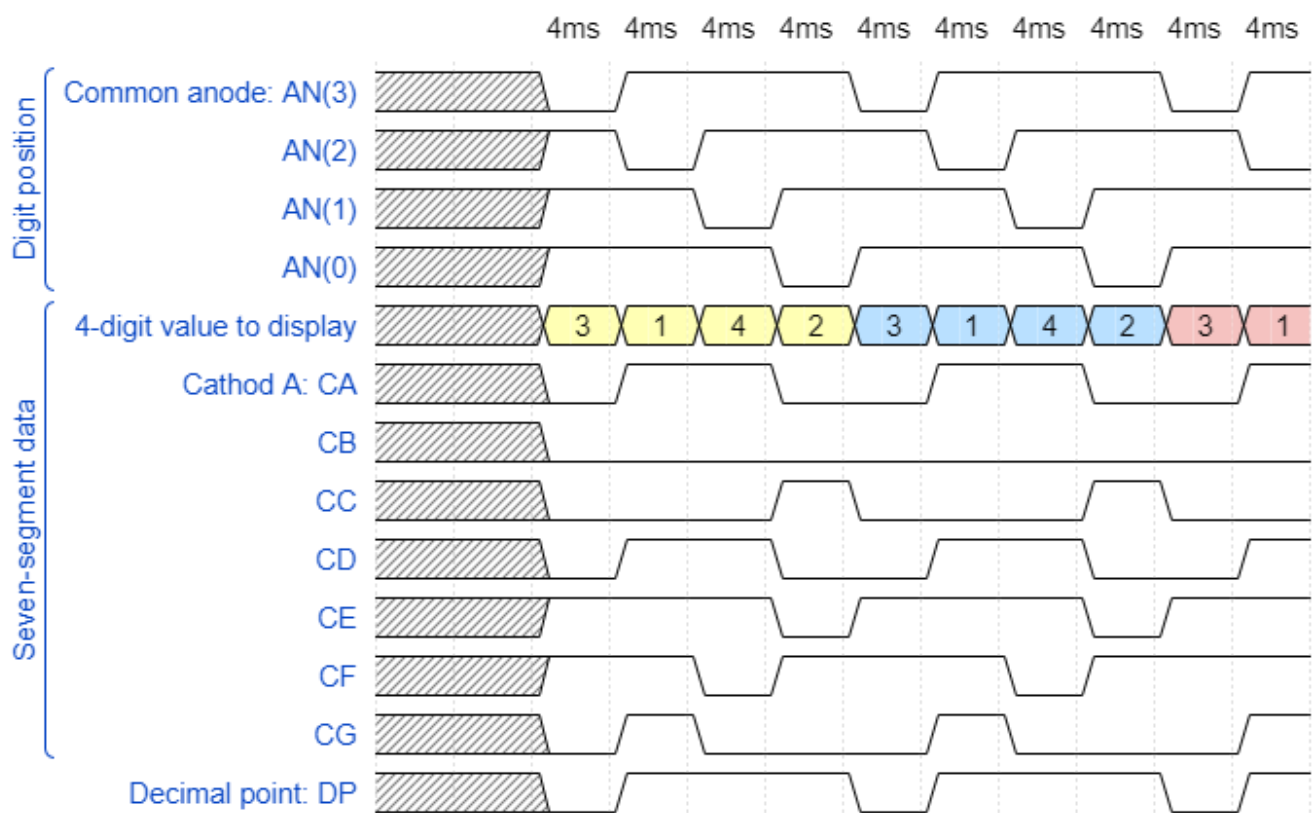


# 06-display\_driver

## My repository

[My git - Tomáš Kříčka, 223283](#)

### 1. Timing diagram figure for displaying value 3.142



### 2. Display driver

VHDL code `p_mux`

```
p_mux : process(s_cnt, data0_i, data1_i, data2_i, data3_i, dp_i)
begin
    case s_cnt is
        when "11" =>
            s_hex <= data3_i;
            dp_o  <= dp_i(3);
            dig_o <= "0111";

        when "10" =>
```

```

        s_hex <= data2_i;
        dp_o  <= dp_i(2);
        dig_o <= "1011";

    when "01" =>
        s_hex <= data1_i;
        dp_o  <= dp_i(1);
        dig_o <= "1101";

    when others =>
        s_hex <= data0_i;
        dp_o  <= dp_i(0);
        dig_o <= "1110";
    end case;
end process p_mux;

```

## VHDL testbench

```

-----
--
-- Template for 4-digit 7-segment display driver testbench.
-- Nexys A7-50T, Vivado v2020.1.1, EDA Playground
--
-- Copyright (c) 2020 Tomas Fryza
-- Dept. of Radio Electronics, Brno University of Technology, Czechia
-- This work is licensed under the terms of the MIT license.
--
-----

library ieee;
use ieee.std_logic_1164.all;

-----
-- Entity declaration for testbench
-----
entity tb_driver_7seg_4digits is
    -- Entity of testbench is always empty
end entity tb_driver_7seg_4digits;

-----
-- Architecture body for testbench
-----
architecture testbench of tb_driver_7seg_4digits is

    -- Local constants
    constant c_CLK_100MHZ_PERIOD : time    := 10 ns;

    --Local signals
    signal s_clk_100MHz : std_logic;

```

```

signal s_clk      : std_logic;
signal s_reset    : std_logic;

signal s_data0_i  : std_logic_vector (4 - 1 downto 0);
signal s_data1_i  : std_logic_vector (4 - 1 downto 0);
signal s_data2_i  : std_logic_vector (4 - 1 downto 0);
signal s_data3_i  : std_logic_vector (4 - 1 downto 0);
signal s_dp_i     : std_logic_vector (4 - 1 downto 0);

signal s_dp_o     : std_logic;
signal s_seg_o    : std_logic_vector (7 - 1 downto 0);
signal s_dig_o    : std_logic_vector (4 - 1 downto 0);

begin
-- Connecting testbench signals with driver_7seg_4digits entity
-- (Unit Under Test)
uut_driver_7seg : entity work.driver_7seg_4digits
    port map(
        clk      => s_clk_100MHz,
        reset    => s_reset,

        data0_i => s_data0_i,
        data1_i => s_data1_i,
        data2_i => s_data2_i,
        data3_i => s_data3_i,

        dp_i     => s_dp_i,
        dp_o     => s_dp_o,
        seg_o    => s_seg_o,
        dig_o    => s_dig_o
    );

-----
-- Clock generation process
-----
p_clk_gen : process
begin
    while now < 750 ns loop                -- 75 periods of 100MHz clock
        s_clk_100MHz <= '0';

        wait for c_CLK_100MHZ_PERIOD / 2;
        s_clk_100MHz <= '1';

        wait for c_CLK_100MHZ_PERIOD / 2;
    end loop;
    wait;
end process p_clk_gen;

-----
-- Reset generation process
-----
p_reset_gen : process
begin

```

```
s_reset <= '0';
wait for 12 ns;

-- Reset activated
s_reset <= '1';
wait for 50 ns;

s_reset <= '0';
wait;
end process p_reset_gen;

-----
-- Data generation process
-----

p_stimulus : process
begin
    report "Start simulation" severity note;

    s_data3_i <= "0011";
    s_data2_i <= "0001";
    s_data1_i <= "0100";
    s_data0_i <= "0010";
    s_dp_i    <= "0111";

    wait for 450ns;


    s_data3_i <= "0110";
    s_data2_i <= "0100";
    s_data1_i <= "0001";
    s_data0_i <= "0010";
    s_dp_i    <= "0111";

    report "End simulation" severity note;
    wait;
end process p_stimulus;


end architecture testbench;
```

## Simulation

Wavefoms for 3.142

 

Wavefoms for 641.2

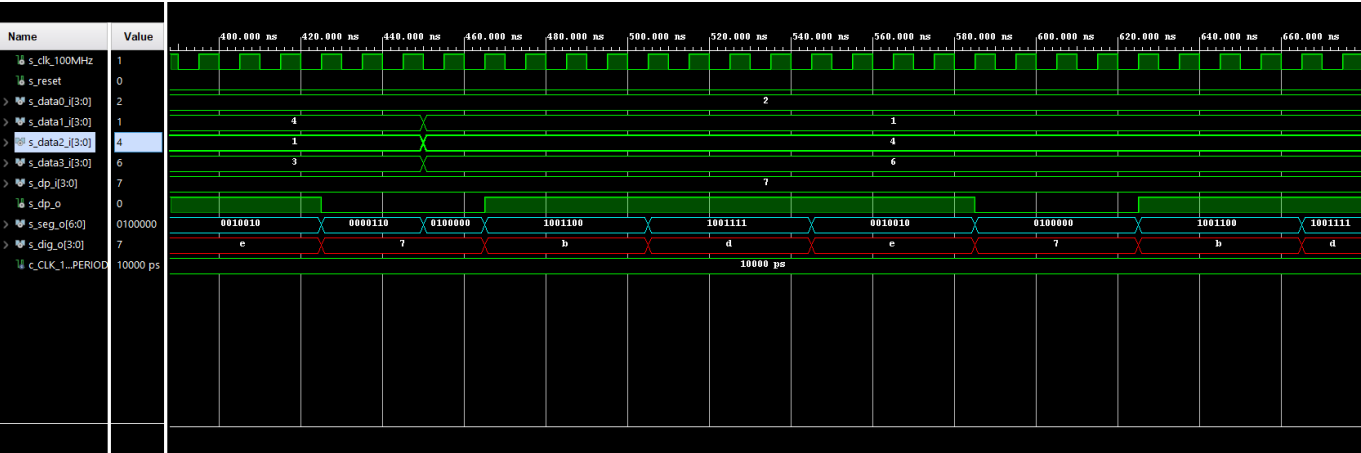

VHDL code **top**

```
architecture Behavioral of top is
    -- No internal signals
begin

    -----
    -- Instance (copy) of driver_7seg_4digits entity
    driver_seg_4 : entity work.driver_7seg_4digits
        port map(
            clk          => CLK100MHZ,
            reset        => BTNC,
            data0_i(3)   => SW(3),
            data0_i(2)   => SW(2),
            data0_i(1)   => SW(1),
            data0_i(0)   => SW(0),

            data1_i(3)   => SW(7),
            data1_i(2)   => SW(6),
            data1_i(1)   => SW(5),
            data1_i(0)   => SW(4),
```

```

    data2_i(3) => SW(11),
    data2_i(2) => SW(10),
    data2_i(1) => SW(9),
    data2_i(0) => SW(8),

    data3_i(3) => SW(15),
    data3_i(2) => SW(14),
    data3_i(1) => SW(13),
    data3_i(0) => SW(12),
    --- WRITE YOUR CODE HERE
    dp_i => "0111",
    dig_o  => AN (4 - 1 downto 0),
    seg_o(0)  => CA,
    dp_o  => DP
    --- WRITE YOUR CODE HERE
);

-- Disconnect the top four digits of the 7-segment display
AN(7 downto 4) <= b"1111";

end architecture Behavioral;

```

## 8-digit driver

### Schema

